

1601/102

1602/102

APPLIED SCIENCE, ELECTRICAL
PRINCIPLES I AND ELECTRONICS

Oct./Nov. 2017

Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

**CRAFT CERTIFICATE IN ELECTRICAL AND ELECTRONIC TECHNOLOGY
(POWER OPTION)
(TELECOMMUNICATION OPTION)**

MODULE I

APPLIED SCIENCE, ELECTRICAL PRINCIPLES I AND ELECTRONICS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Non-programmable scientific calculator;

Drawing instruments.

*This paper consists of **THREE** sections; **A**, **B** and **C**.*

*Answer **ONE** question from section **A** and **TWO** questions each from section **B** and **C**.*

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

Take: $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

This paper consists of 6 printed pages.

**Candidates should check the question paper to ascertain that
all the pages are printed as indicated and that no questions are missing.**

SECTION A: APPLIED SCIENCE

Answer any **ONE** question from this section.

1. (a) (i) List **two** properties of acids.
 - (ii) Differentiate between the following terms as used in chemistry:
 - (I) atomic number and mass number;
 - (II) period and group. (5 marks)

*Period: The electrons increases across the table from left to right
Group: The energy levels increase from top downwards.*
 - (b) (i) State **two** forms of heat transfer.
*Radiation
Convectional*
 - (ii) A steel boiler of mass 12 kg has 25 kg of water at 98° C. When 70 kg of water at 16° C was added to the boiler, a steady temperature of 38.5° C was obtained. The specific heat capacity of water is 4200 J/kg K. Determine the specific heat capacity of steel boiler. Assume heat loss to the surrounding is negligible. (7 marks)
- $$\frac{4200 \times 25 \times (98 - 38.5)}{70 \times (38.5 - 16)} = S_{AC}$$
- (c) (i) State the energy conversion when:
 - (I) a simple pendulum bob is made to swing;
 - (II) solar battery is used to light a filament bulb.

*AC to DC
DC to AC*
 - (ii) A simple d.c generator produces 12000 joules of energy per minute. Determine its power. (5 marks)
- $$P = \frac{12000}{60} = 200 \text{ watts}$$
- (d) Explain how a glass rod acquires electrostatic charges when rubbed against fur. (3 marks)

2. (a) (i) Define:
 - (I) density;
 - (II) relative density.
- (ii) The relative density of dam water is 1.13. Calculate its density in kg/m³. (3 marks)
- (b) (i) State **three** properties of electromagnetic waves.
- (ii) Draw a labelled diagram of the electromagnetic spectrum. (6 marks)
- (c) (i) Define the isothermal process.
- (ii) Sketch graphs to represent each of the following:
 - (I) Boyle's law;
 - (II) Charles's law. (5 marks)

- (d) A convex lens of focal length 10 cm is used to magnify an object placed at a distance 15 cm from it. Determine the:

- (i) image distance;
(ii) magnification.

(6 marks)

SECTION B: ELECTRICAL PRINCIPLES I

Answer any **TWO** questions from this section.

3. (a) State two:

- (i) advantages of an alkaline cell over lead acid cell.
(ii) indications of a fully charged lead-acid cell.

(4 marks)

- (b) Draw a labelled diagram of a leclanche dry cell.

(5 marks)

- (c) Define the following terms as used in electrostatics:

- (i) electric flux density;
(ii) relative permittivity.

(4 marks)

- (d) Figure 1 shows a capacitive circuit:

- (i) Show that the potential difference across C_1 is given by:

$$V_1 = \left(\frac{C_2}{C_1 + C_2} \right) V$$

- (ii) Determine the capacitance of capacitor C_2 if $C_1 = 20 \mu\text{F}$ and total capacitance is $12 \mu\text{F}$.

(7 marks)

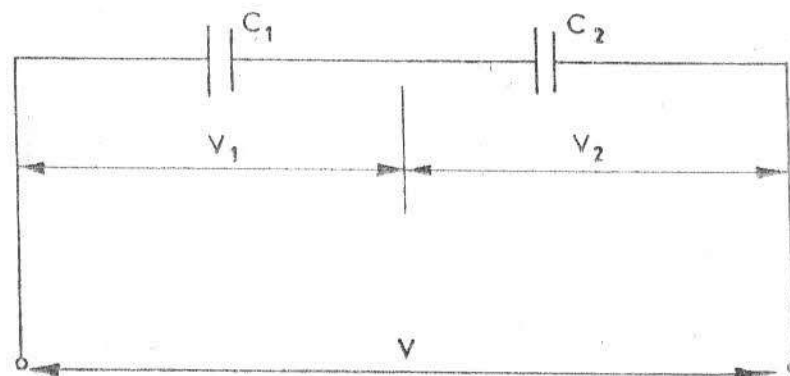


Fig. 1

1601/102

1602/102

Oct./Nov. 2017

30uf

250 450 150 150 150

4. (a) State:
- three** factors that determine the force on a current carrying conductor in a magnetic field.
 - Faraday's laws of electromagnetic induction. (5 marks)
- (b) Outline **four** factors which affect the inductance of an inductor. (4 marks)
- (c) A flux of 20 mwb links with a 1200 turns coil when a current of 2A passes through the coil. Determine the:
- inductance of the coil;
 - energy stored in the magnetic field;
 - average emf induced in the coil if current falls to zero in 120 ms. (7 marks)
- (d) Sketch the following transformer construction:
- core type;
 - shell type. (4 marks)
5. (a) State:
- three** effects of an electric current and **one** application of each;
 - two** types of resistors. (5 marks)
- (b) A wire of length 6 cm and cross-sectional area of 4 mm^2 has a resistance of 0.12Ω . If the wire is drawn out until its cross sectional area is 2 mm^2 , determine the new resistance of the wire. (4 marks)
- (c) Figure 2 shows an electric circuit. Show that by current division; $I_1 = \left(\frac{I R_2}{R_1 + R_2} \right)$. (5 marks)

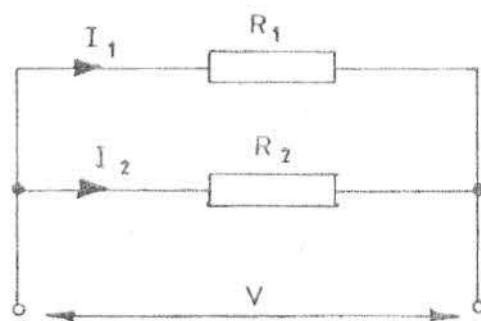


Fig. 2

$$I_1 R_1 + I_2 R_2 = I_2 R_2$$

$$I_1 R_1 + I_2 R_2 = V$$

$$I_1 R_1 = V - I_2 R_2$$

$$I_1 = \frac{V - I_2 R_2}{R_1}$$

$$I_1 = \frac{I_2 R_2}{R_1} + \frac{V}{R_1}$$

$$I_1 = \frac{I_2 R_2}{R_1} + \frac{I_1 (R_1 + R_2)}{R_1}$$

$$I_1 R_1 = \frac{I_2 R_2}{R_1} R_1 + \frac{I_1 (R_1 + R_2)}{R_1} R_1$$

$$I_1 R_1 = I_2 R_2 + I_1 (R_1 + R_2)$$

$$I_1 R_1 - I_1 (R_1 + R_2) = I_2 R_2$$

$$I_1 R_1 - I_1 R_1 - I_1 R_2 = I_2 R_2$$

$$-I_1 R_2 = I_2 R_2$$

$$I_1 = -I_2$$

$$I_1 = \frac{I_2 R_2}{R_1 + R_2}$$

$$I_1 = \frac{I R_2}{R_1 + R_2}$$

- (d) Figure 3 shows an electric circuit. When switch S is closed, the reading on the voltmeter $V = 40 \text{ V}$ and $V_2 = 15 \text{ V}$. Determine the:
- reading on the ammeter;
 - value of R_2 .

(6 marks)

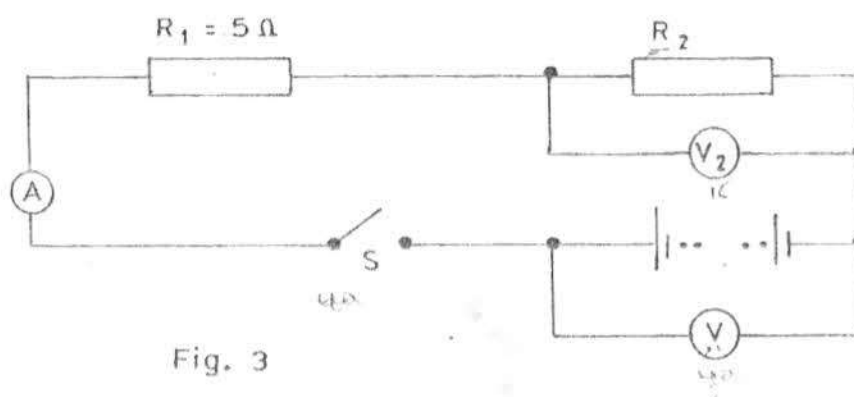


Fig. 3

SECTION C: ELECTRONICS

Answer any **TWO** questions from this section.

- Explain the term 'doping' as used in semi conductors. (2 marks)
 - With aid of a diagram, describe the operation of a NPN bipolar junction transistor. (8 marks)
 - Outline **three** tests that may be carried out on electronic components. (3 marks)
 - With aid of circuit diagram and voltage waveforms, explain the operation of a half wave rectifier circuit. (7 marks)
- State **four** types of negative feedback used in electronic amplifiers.
 - An amplifier has internal gain of 200. Determine the new gain if a negative feedback with feedback factor of 0.2 is introduced. (8 marks)

- (b) (i) Determine the decimal number represented by $(0.10111000)_2$.
 (ii) Obtain decimal equivalent of hexadecimal number $(3A.3F)_{16}$.
 (iii) Add binary numbers 1111 and 1100.

$$\begin{array}{r} 0+0=0 \\ 1+0=1 \\ 0+1=1 \\ 1+1=0 \end{array}$$

$$\begin{array}{r} 00010111 \\ 01101100 \\ \hline 01111100 \\ 7 \end{array}$$

(8 marks)

- (c) Simplify the following boolean expression:
 $(AB + C)(AB)$.

(4 marks)

8. (a) (i) State **two** types of logic families.

- (ii) Figure 4 shows a three input OR gate. Draw its truth table.

(10 marks)

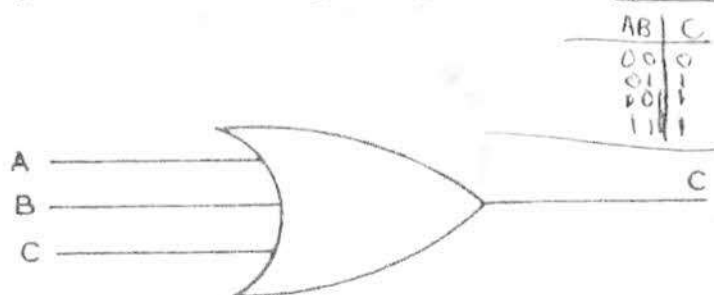


Fig. 4

- (b) Draw the:

- (i) diagram of a T-type flip-flop; $T \rightarrow \text{flip-flop} \rightarrow \bar{T}$

- (ii) truth table of the flip-flop in b (i).

(5 marks)

- (c) (i) Sketch the ideal response curve of a low pass filter.

- (ii) Draw an R-C high pass filter network.

(5 marks)

THIS IS THE LAST PRINTED PAGE.

$$\begin{array}{r} 1111 \\ 1111 \\ 0110 \\ \hline 0410 \\ 0111 \end{array}$$

$$\begin{array}{r} 1100 \\ 0110 \\ 0010 \\ \hline 0011 \end{array}$$