1521/205
1601/205
ELECTRICAL INSTALLATION II,
ESTIMATING AND TENDERING,
INDUSTRIAL MACHINES
AND CONTROLS
Oct./Nov. 2017
Time: 3 hours



### THE KENYA NATIONAL EXAMINATIONS COUNCIL

# CRAFT CERTIFICATE IN ELECTRICAL AND ELECTRONIC TECHNOLOGY (POWER OPTION) MODULE II

ELECTRICAL INSTALLATION II, ESTIMATING AND TENDERING, INDUSTRIAL MACHINES AND CONTROLS

3 hours

#### INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

Answer booklet;

Mathematical tables/Scientific calculator.

This paper consists of EIGHT questions in TWO sections: A and B.

Answer FIVE questions choosing THREE questions from section A and TWO questions from section B.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated.

Candidates should answer the questions in English.

This paper consists of 7 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

© 2017 The Kenya National Examinations Council

Turn over

## SECTION A


Answer any THREE questions from this section.

- 1. (a) (i) Define 'Power-factor'.
  - (ii) Illustrate how a delta capacitor bank is connected to correct the power-factor of a three phase induction motor.

(6 marks)

- (b) State two factors which determine the selection of a synchronous motor for power factor correction. (2 marks)
- (e) (i) A power consumer has an annual energy consumption of 860,000 units and a maximum load of 450 kW at 0.75 power factor lagging. The tariff is Sh. 6 per annum of KVA of maximum demand plus Sh. 0.50 per unit. Determine the annual charge of electricity.
  - (ii) Figure 1 shows load curves for consumers x and y. With reason, state between the two consumers who has a better load factor.

(12 marks)

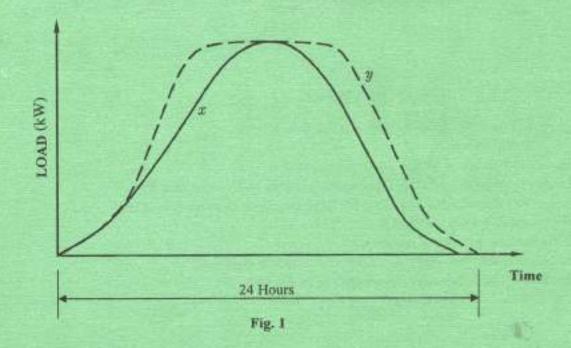

- 2. (a) (i) State three characteristics of M.I.C.S cables.
  - (ii) Outline two conditions observed when installing a catenary wiring system.

(5 marks)

- (b) Describe the following wiring systems:
  - (i) trunking;

ducting. (4 marks)

(c) Use table 1 provided to determine the approximate size of trunking necessary to accommodate 25 cables of 1/1.78 mm size and 7 cables of 7/1.70 size, all PVC insulated. (Assume a space factor of 45%). (6 marks)

Table 1

(iii)

| Cable size | Fa  | ctor   | Connector | Trunking |  |
|------------|-----|--------|-----------|----------|--|
|            | PVC | Rubber | Capacity  |          |  |
| 1/1.13     | 14  | 13     | 1000      | 38 x 38  |  |
| 1/1.38     | 18  | 17     | 1350      | 50 x 38  |  |
| 7/1.35     | 51  | 58     | 3600      | 100 x 50 |  |
| 7/1.70     | 71  | 74     | 4050      | 75 x 75  |  |

(d) Draw a labelled wiring diagram of a three-phase supply system feeding a three phase motor and one single phase domestic consumer. (5 marks)

- 3. (a) Draw a circuit diagram of a d.c shunt motor connected to drive a load. (4 marks)
  - (b) Figure 2 shows a contactor control circuit of a d.c. motor:
    - (i) State the purpose of the circuit.
    - (ii) Explain the operation of the circuit.

(6 marks)

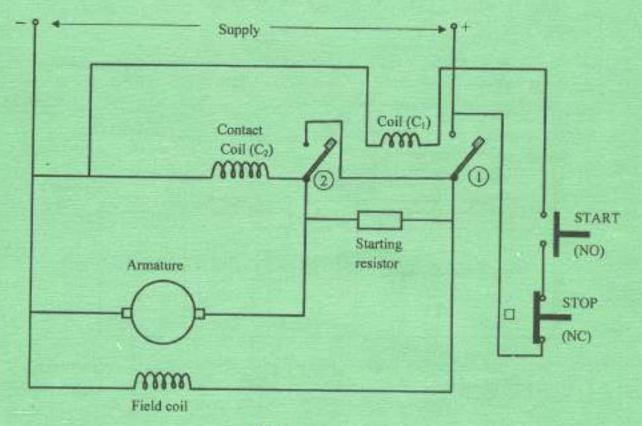


Fig. 2

- (c) (i) State three IEE regulation requirements for electric motors.
  - Outline the procedure for carrying out routine inspection and tests on a three-phase induction motor.

(10 marks)

4. (a) Define an instrumentation system. - 1) = 20 | Value = 20 | 4.

(3 marks)

- (b) (i) Explain the function of a data logger when used in instrumentation systems.
  - (ii) State five component parts of a data logger.

(8 marks)

(c) List four advantages of using a motor control panel.


(4 marks)

(d) Explain the operation of a three phase induction motor.

(5 marks)

1521/205 Oct./Nov. 2017 1601/205

-

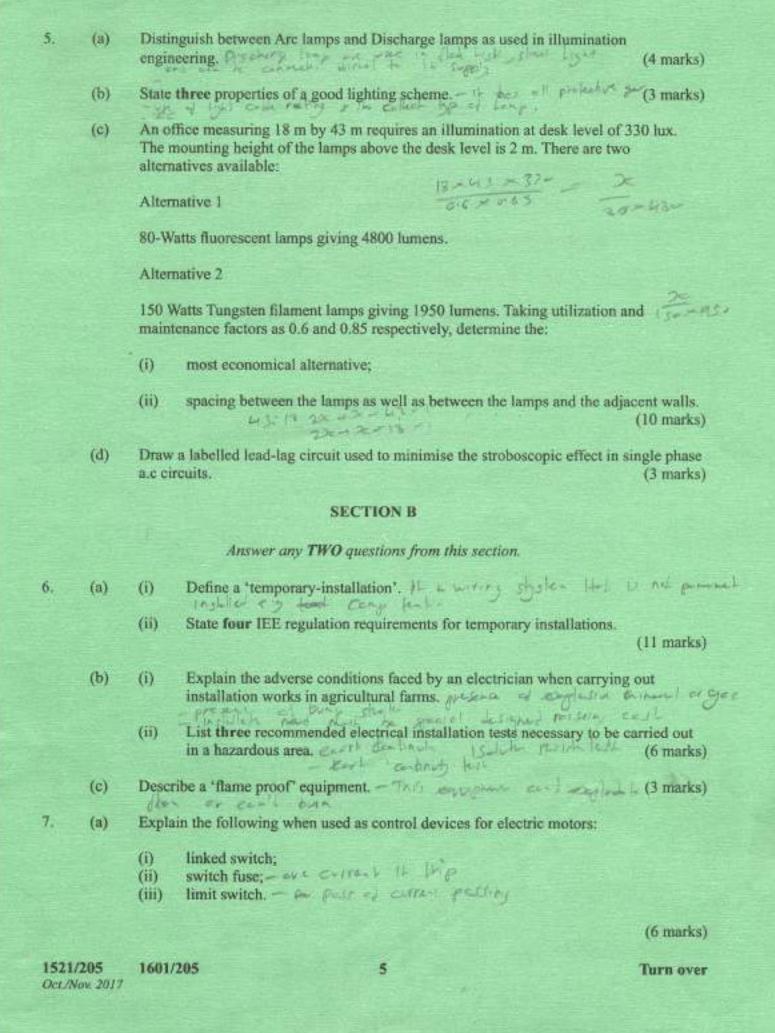

- (b) State:
  - (i) three advantages of using Programmable Logic Controllers (PLC) over electrical relays for industrial motor control;
  - (ii) two types of 'contacts' used in PLC.

(5 marks)

(c) Two motors M<sub>1</sub> and M<sub>2</sub> are such that motor M<sub>1</sub> is started by pressing switch I<sub>2</sub> while motor M<sub>2</sub> is started by pressing switch I<sub>3</sub>. When motor M<sub>2</sub> starts, motor M<sub>3</sub> should remain off. Draw the ladder diagram for this operation. (9 marks)

Importante of an photonium

- 8. (a) Explain the importance of the following elements of estimating:

  - (ii) site visits and programme; de to me he had be for the size of the size
  - (iii) regulations.

(6 marks)

- (b) (i) State four factors that affect the pricing of an estimate.
  - (ii) Explain the purpose of Bills of Quantities in an estimate.

(6 marks)

7 7 4 7

0 = 34

1 00 12

2 = MAL

(c) Figure 3 shows a pictorial chart of progress in project development of electrical wiring works. Summarise the status of the project. (8 marks)

## Room Numbers

| FLOOR           | 1 | 2                 | 3                   | 4                       | 5                 | 6                 | 7                 | 8                 |
|-----------------|---|-------------------|---------------------|-------------------------|-------------------|-------------------|-------------------|-------------------|
| Ground          | X | X                 | X                   | $\searrow$              | $\searrow$        | $\times$          | $\times$          | $\langle$         |
| 14              |   | $\Leftrightarrow$ | $\Leftrightarrow$   | $\Leftrightarrow$       | $\Leftrightarrow$ | $\Leftrightarrow$ | $\Leftrightarrow$ | $\Leftrightarrow$ |
| 2°d             |   |                   |                     | $\langle \cdot \rangle$ |                   |                   |                   |                   |
| 3 <sup>18</sup> |   |                   |                     |                         | 1                 |                   |                   |                   |
| 46              |   |                   |                     | 1                       |                   |                   |                   |                   |
| 5th -           |   |                   |                     |                         |                   |                   |                   |                   |
| 6 <sup>th</sup> |   |                   |                     |                         |                   |                   |                   |                   |
| 7°              |   |                   | THE PERSON NAMED IN |                         |                   |                   |                   |                   |

Fig. 3

| Key |   | 1         | しょ   |
|-----|---|-----------|------|
|     | Conduit laid  | 4         | mes* |
|     | Conduit laid and wiring completed   |           |      |
| X   | Conduit laid, wiring completed and accessories fitted                       |           |      |
| X   | Conduit laid, wiring completed, accessori instalation inspected and testsed | es fitted | i,   |
|     | No work carried out   |           |      |

THIS IS THE LAST PRINTED PAGE.